

CSE 331 Computer Organization
Homework 2
Hamza Yoğurtcuoğlu - 171044086
10 October , 2018

module four_to_one_mux(mux_output,a,b,c,d,selector_one,selector_two)

This mux is needed for Opcode0.1 that needs each 32 bits. There are four input and 2 selector inputs and 1 output.

module two_to_one_mux (mux_output,a,b,selector)

This module is used Opcode2 and rightshift and leftshift. There are 2 input and 1 selector input and 1 output.

**module alu32 (R ,S, A , B ,zerocontrol,overflow,
zerocontrolSub,overflowSub,zerocontrolRight
,zerocontrolLeft,zerocontrolNor,
zerocontrolAnd,zerocontrolOr,zerocontrolXor)**

All other models are called in here . There are 64 mux (4:1) for opcode1,0 and 32 mux (2:1) for opcode2 . Because we create a result according of selector opcodes.

module and_A_B (and_A_B, A , B,zerocontrolAnd)

32 bit A and 32 bit B are operating with and gates.

module or_A_B (or_A_B, A , B,zerocontrolOr)

32 bit A and 32 bit B are operating with or gates.

module full_adder(sum,cin_plus_one,cin,a,b)

This module is just for 1 bit add. Im using for sub ,add instructions .

module add_A_B(add_R,A,B,zerocontrol,overflow)

Each carry out bit and A and B bit are added by full_adder module. We can check overflow and Implementation of zero.

module xor_A_B(xor_R , A , B,zerocontrolXor)

32 bit A and 32 bit B are operating with xor gates.

module sub_A_B(sub_R,A,B,zerocontrolSub,overflowSub)

Firstly , We are getting two complement's of B number . Then Each carry out bit and A and B bit are added by full_adder module. We can check overflow and Implementation of zero.

module rightAr_A_B(rightAr_R,A,B,zerocontrolRight)

At first just 1 bit shift to right with through 2:1 mux . But we need to put most significant bit digit of the number to empty left field . Then 2 bit ,4bit,8bit,16bit then finish checking.Because if there is a one bit B[5]-[31]. All result is 000.....000

module leftLo_A_B(leftLo_R,A,B,zerocontrolLeft)

Firstly , just 1 bit shift to left with through 2:1 mux . But we need to put '0' to empty right field .Then 2 bit ,4bit,8bit,16bit then finish checking.Because if there is a one bit B[5]-[31]. All result is 000.....000

module nor_A_B(nor_R,A,B,zerocontrolNor)

32 bit A and 32 bit B are operating with nor gates.

NOTE : ALL OVERFLOW AND IMPLEMENTATION OF ZERO IS CHECKED.

```
A = 11111100000000000100000010001001 B = 00000000000000000000000000001111 Result = 00000000000000000000000000001001 Select : 000
ZeroControl:0, Overflow:0, Carry_Out:0
A = 111111000000000000100000010001001 B = 00000000000000000000000000001111 Result = 11111100000000000100000010001111 Select : 001
ZeroControl:0, Overflow:0, Carry_Out:0
A = 111111000000000000100000010001001 B = 00000000000000000000000000001111 Result = 11111100000000000100000010011000 Select : 010
ZeroControl:0, Overflow:0, Carry_Out:0
A = 111111000000000000100000010001001 B = 00000000000000000000000000001111 Result = 11111100000000000100000010000110 Select : 011
ZeroControl:0, Overflow:0, Carry_Out:0
A = 111111000000000000100000010001001 B = 00000000000000000000000000001111 Result = 11111100000000000100000001111010 Select : 100
ZeroControl:0, Overflow:0, Carry_Out:1
A = 111111000000000000100000010001001 B = 00000000000000000000000000001111 Result = 11111111111111111111100000000000 Select : 101
ZeroControl:0, Overflow:0, Carry_Out:1
A = 111111000000000000100000010001001 B = 00000000000000000000000000001111 Result = 00100000010001001000000000000000 Select : 110
ZeroControl:0, Overflow:0, Carry_Out:1
A = 111111000000000000100000010001001 B = 00000000000000000000000000001111 Result = 0000001111111111101111101110000 Select : 111
ZeroControl:0, Overflow:0, Carry_Out:1


A = 111111000000000100000111111101001 B = 10000000100100001000111111010011 Result = 100000000000000000000111111000001 Select : 000
ZeroControl:0, Overflow:1, Carry_Out:1
A = 111111000000000100000111111101001 B = 10000000100100001000111111010011 Result = 1111110010010010100011111111011 Select : 001
ZeroControl:0, Overflow:1, Carry_Out:1
A = 111111000000000100000111111101001 B = 10000000100100001000111111010011 Result = 0111110010010010100111110111100 Select : 010
ZeroControl:0, Overflow:1, Carry_Out:1
A = 111111000000000100000111111101001 B = 10000000100100001000111111010011 Result = 01111100100100101000000000111010 Select : 011
ZeroControl:0, Overflow:1, Carry_Out:1
A = 111111000000000100000111111101001 B = 10000000100100001000111111010011 Result = 0111011011100011000000000010110 Select : 100
ZeroControl:0, Overflow:0, Carry_Out:1
A = 111111000000000100000111111101001 B = 10000000100100001000111111010011 Result = 00000000000000000000000000000000 Select : 101
ZeroControl:1, Overflow:0, Carry_Out:1
A = 111111000000000100000111111101001 B = 10000000100100001000111111010011 Result = 00000000000000000000000000000000 Select : 110
ZeroControl:1, Overflow:0, Carry_Out:1
A = 111111000000000100000111111101001 B = 10000000100100001000111111010011 Result = 00000011011011010111000000000100 Select : 111
ZeroControl:0, Overflow:0, Carry_Out:1

A = 00000100001111111111111111111111 B = 00000100001111111111111111111111 Result = 00000100001111111111111111111111 Select : 000
ZeroControl:0, Overflow:0, Carry_Out:0
A = 00000100001111111111111111111111 B = 00000100001111111111111111111111 Result = 00000100001111111111111111111111 Select : 001
ZeroControl:0, Overflow:0, Carry_Out:0
A = 00000100001111111111111111111111 B = 00000100001111111111111111111111 Result = 00001000011111111111111111111110 Select : 010
ZeroControl:0, Overflow:0, Carry_Out:0
A = 00000100001111111111111111111111 B = 00000100001111111111111111111111 Result = 00000000000000000000000000000000 Select : 011
ZeroControl:1, Overflow:0, Carry_Out:0
A = 00000100001111111111111111111111 B = 00000100001111111111111111111111 Result = 00000000000000000000000000000000 Select : 100
ZeroControl:1, Overflow:0, Carry_Out:1
A = 00000100001111111111111111111111 B = 00000100001111111111111111111111 Result = 00000000000000000000000000000000 Select : 101
ZeroControl:1, Overflow:0, Carry_Out:1
A = 00000100001111111111111111111111 B = 00000100001111111111111111111111 Result = 00000000000000000000000000000000 Select : 110
ZeroControl:1, Overflow:0, Carry_Out:1
A = 00000100001111111111111111111111 B = 00000100001111111111111111111111 Result = 11111011110000000000000000000000 Select : 111
ZeroControl:0, Overflow:0, Carry_Out:1
```


ALU-32 BIT

Hamza yagurtcuoglu
171044086


32 Bit ALU MODULE (ALU32)

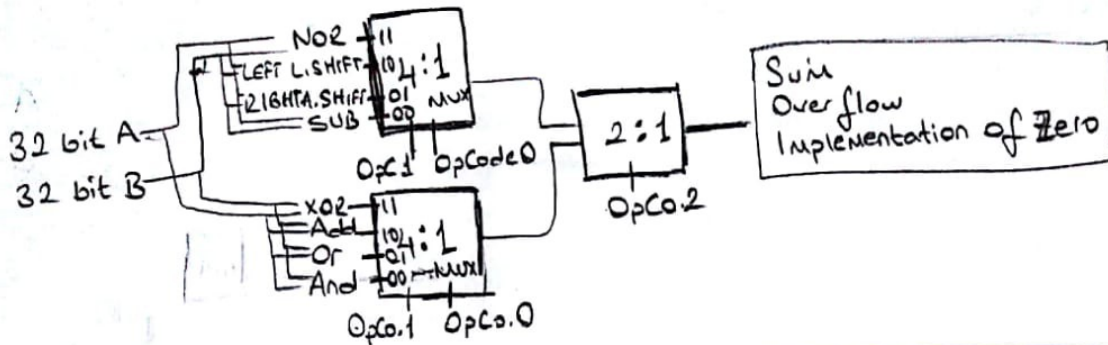


NOR OPERATION (Module)

 

AND MODULE

 


OR MODULE

 


XOR MODULE




ADD MODULE

 

FULL ADDER MODULE

 


Implementation of Zero

 



NOT ALL MODULE HAVE Imp. of Zero Control

RIGHT SHIFT ARITHMETIC MODULE

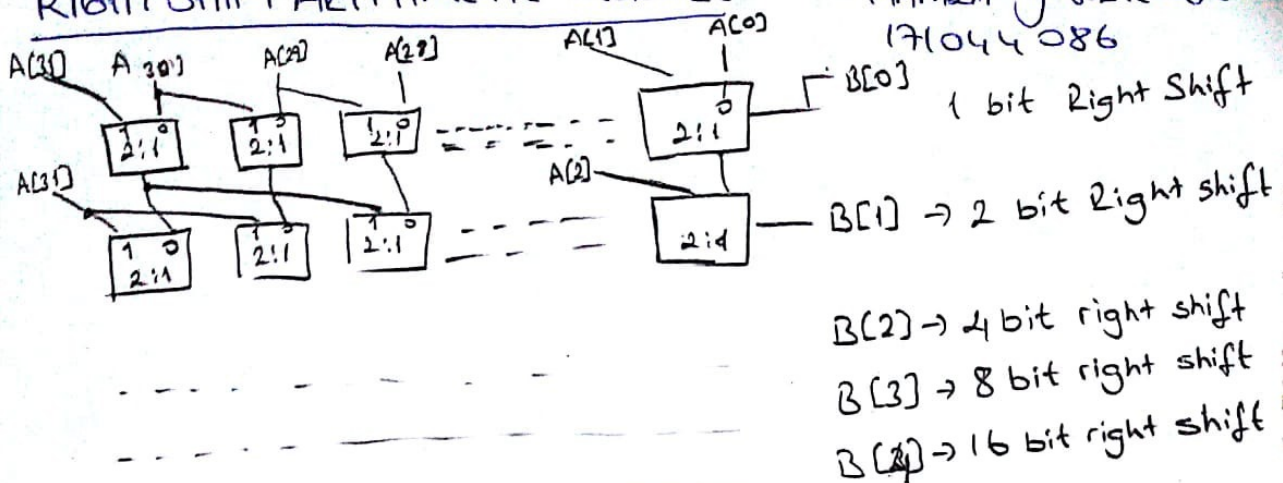


Box: we put most significant digit of number to empty field.

LEFT LOGIC SHIFT

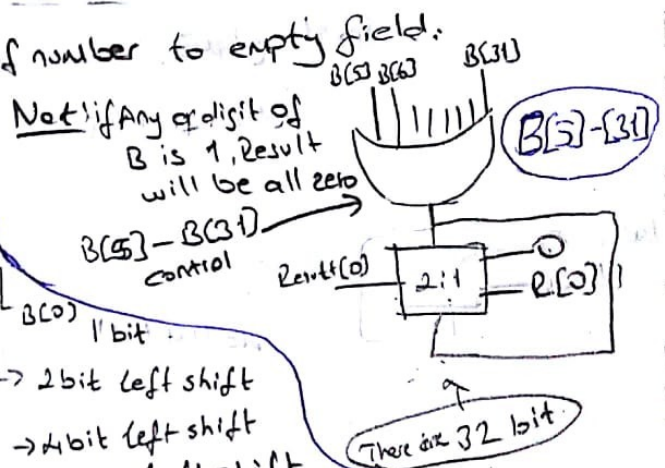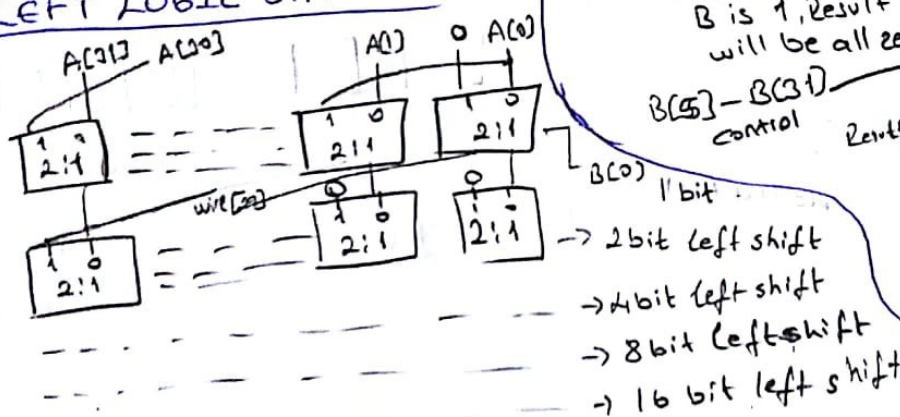

Not! we put 0 bit to empty field and we control B[5] to B[31] with above OR and mux design.


SUB-MODULE

 

Not!
Then we need to 1 for two's complement and

Other side add module same

4:1 Mux

 

2:1 Mux

